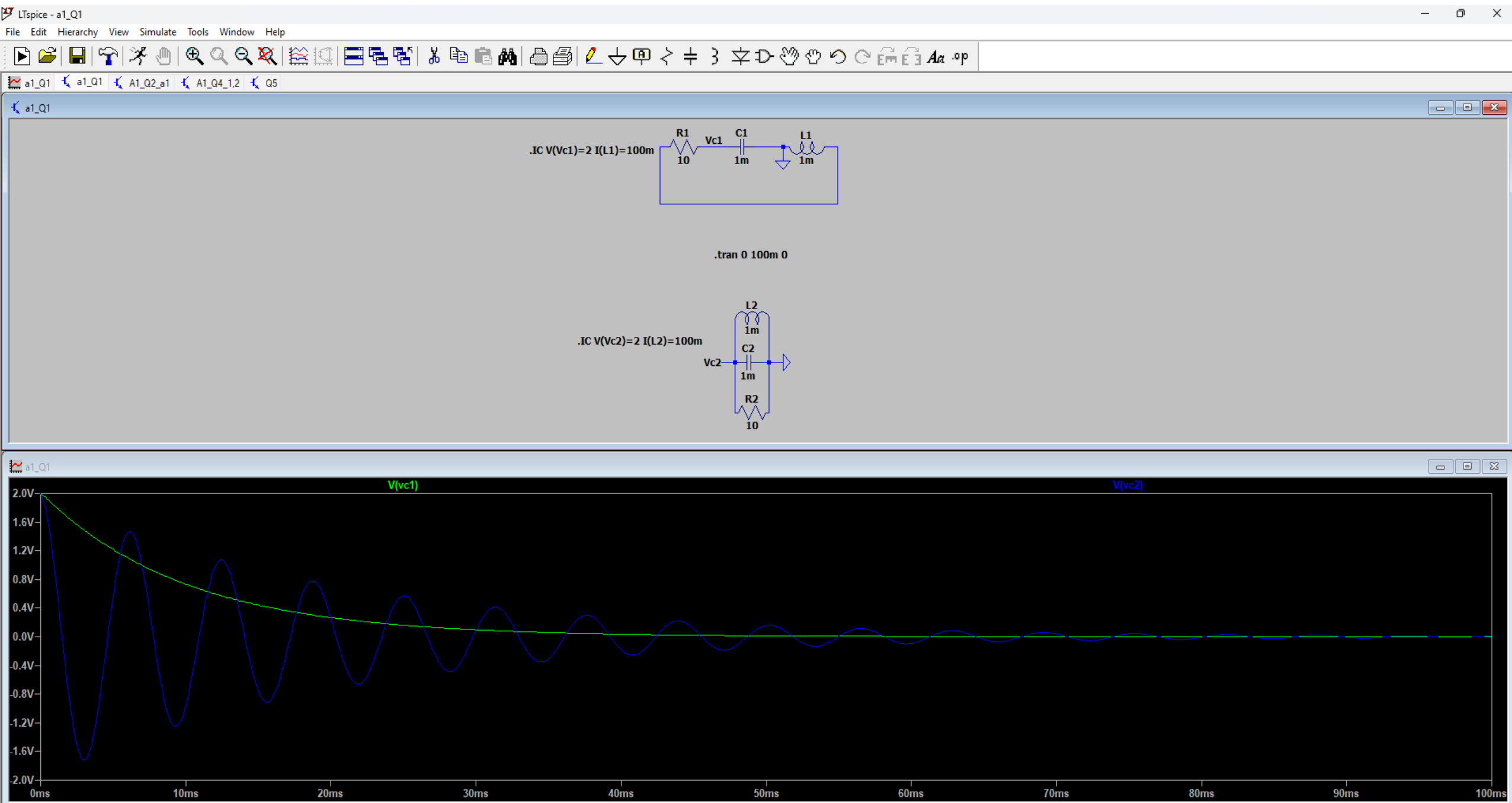


Assignment-01

EE1200

Jay Vikrant
EE22BTECH11025

Q1a,b)



Q1a,b)

for series RLC Circuit, Damping Coefficient(α) = $R/2L = 5000$ Hz

The Natural Frequency(ω_o) = $1/\sqrt{LC} = 1000$ Hz

So, the Damping Factor = $\alpha/\omega_o = R/2 \sqrt{C/L} = 5$

As, $\alpha > \omega_o$, it is over-damped. Overdamped cases don't oscillate.

So, it does not have a Damping Frequency.

for parallel RLC Circuit, the Damping Coefficient (α) = $1/2RC = 50$ Hz







The Natural Frequency (ω_o) = $1/\sqrt{LC} = 1000$ Hz

So, the Damping Factor = $\alpha/\omega_o = 1/2R \sqrt{L/C} = 0.05$

As, $\alpha < \omega_o$, it is underdamped. So, it oscillates.

The Damping Frequency (ω_d) = $\sqrt{\omega_o^2 - \alpha^2} = 999$ Hz

Q2) i-a,b,c

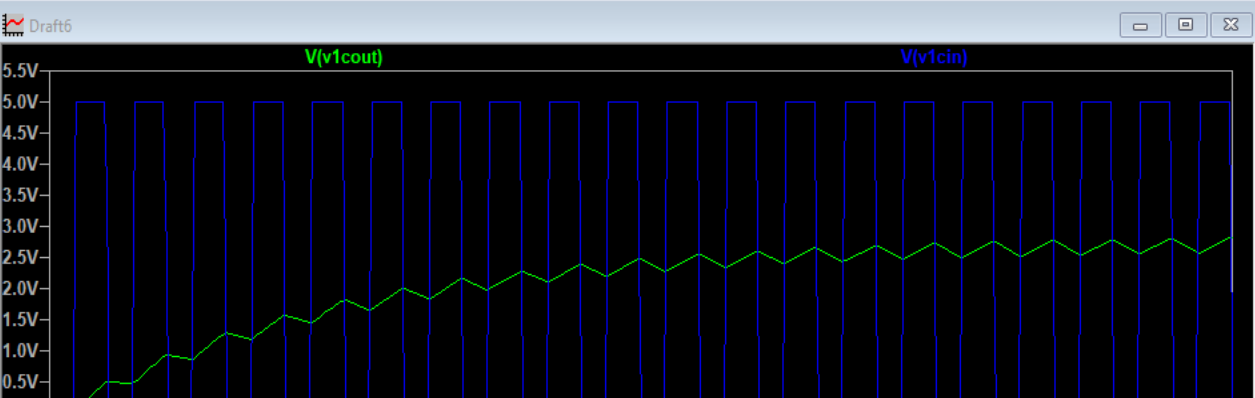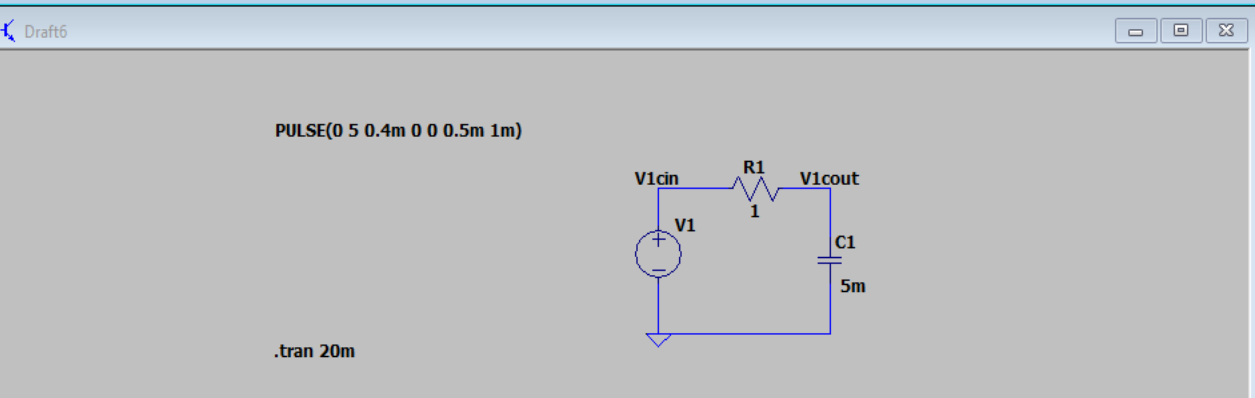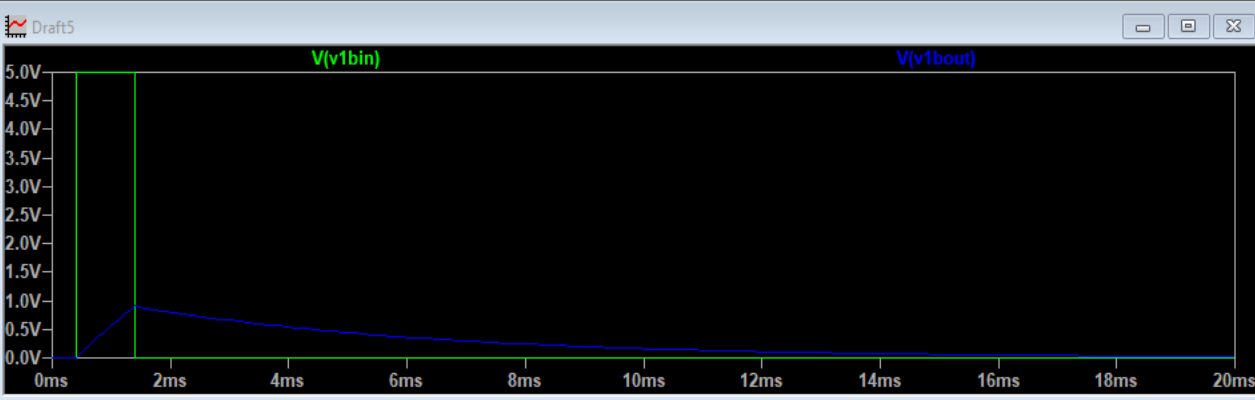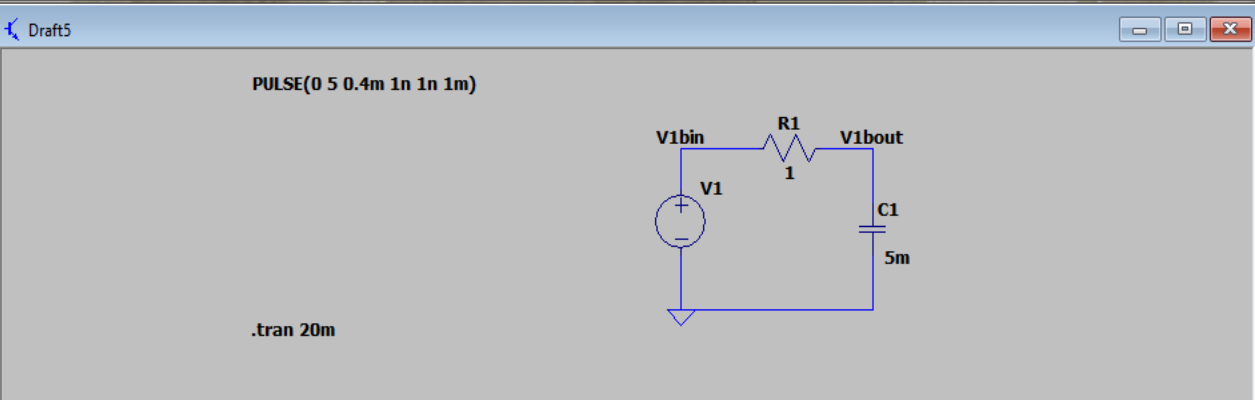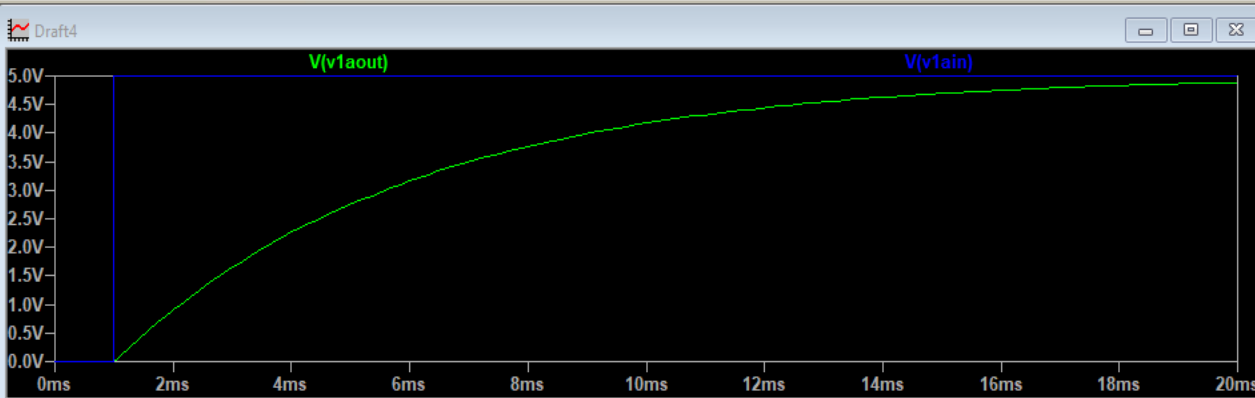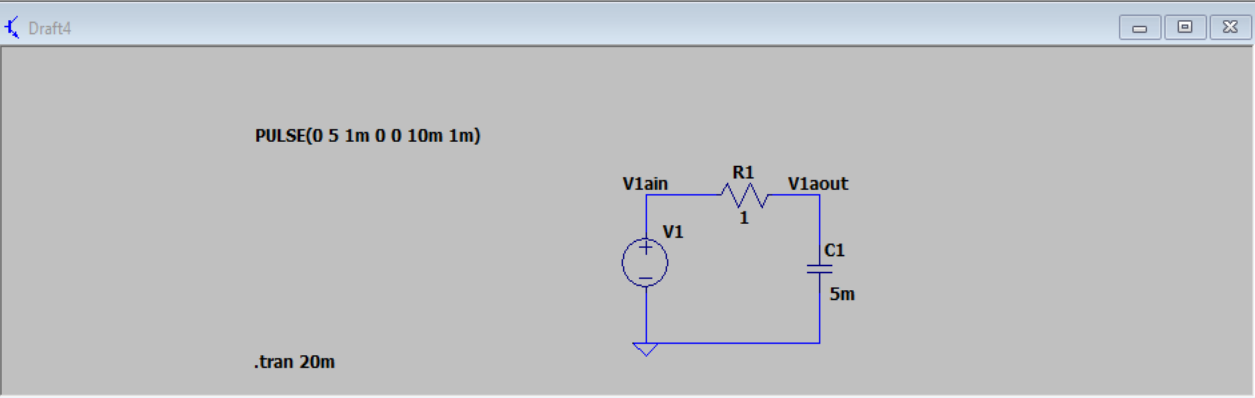

Q2) i-a,b,c

i-a)

The input voltage is a unit step function,

The capacitor voltage spikes when the function takes the value 5 V , it charges the capacitor to a steady state resulting in an almost constant voltage

i-b)

The input voltage is a square pulse,







Square pulse input does not allow capacitor to reach max voltage due to short ON time. Capacitor charges to intermediate value and discharges, losing energy through resistor.

i-c)

The input voltage is infinite number of square wave,

The square pulses with 5V peak and 0V minimum charge a capacitor through a resistor, causing repeated charging and discharging. Eventually, the capacitor reaches a steady state with constant max and min voltages.

Q2) ii-a,b,c

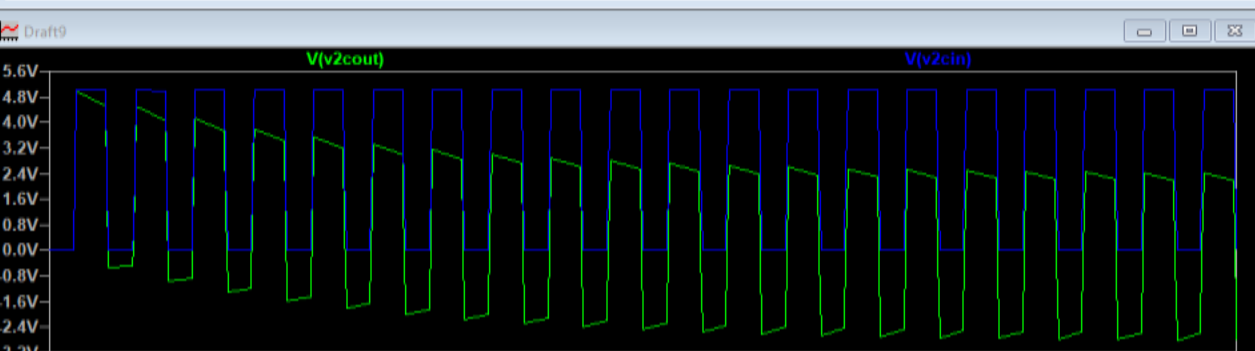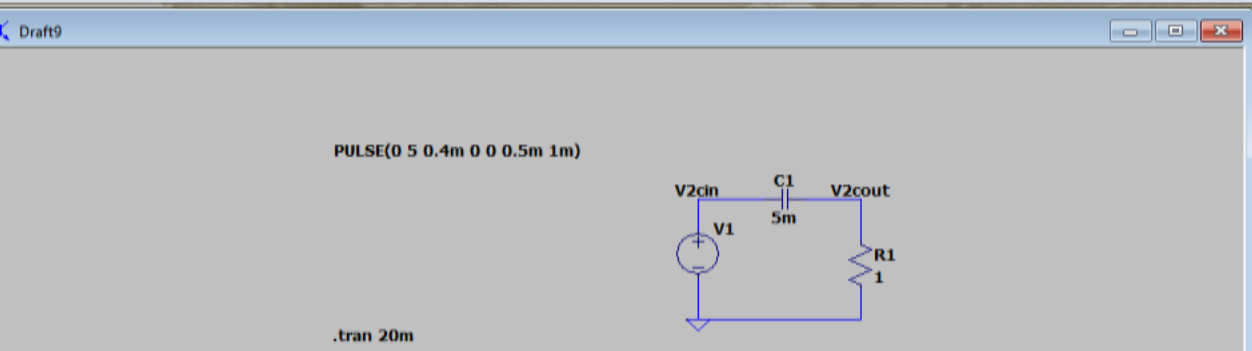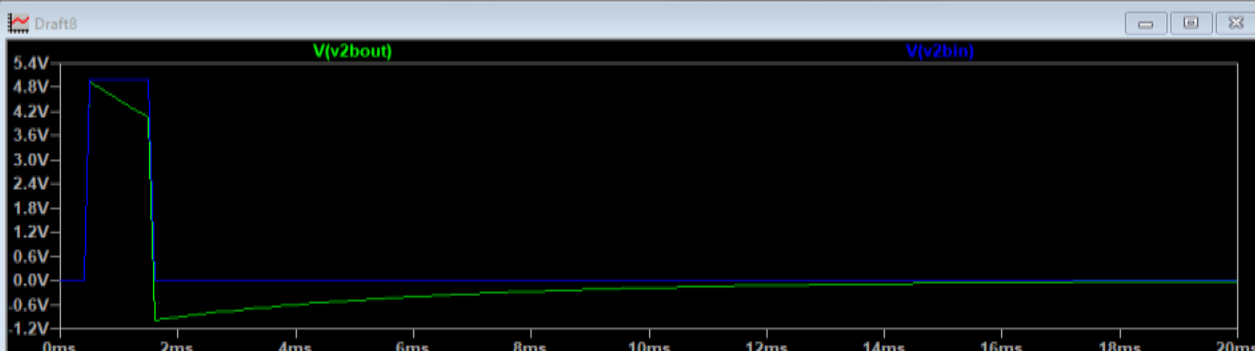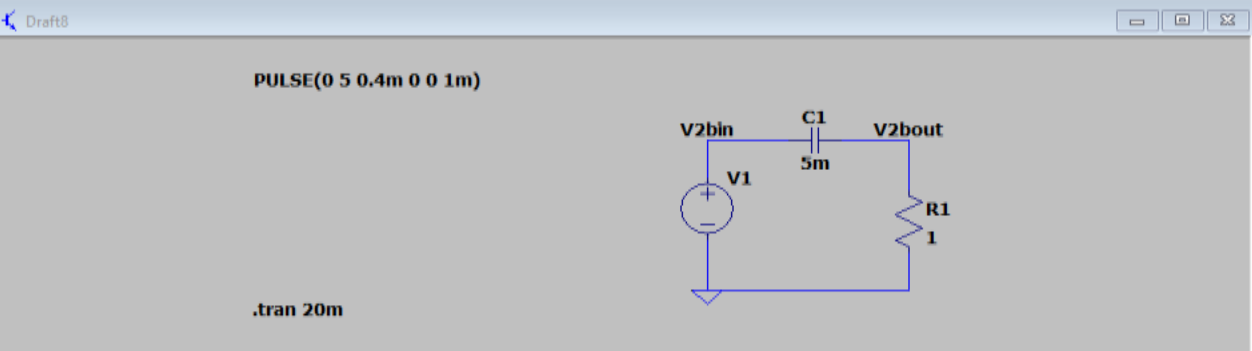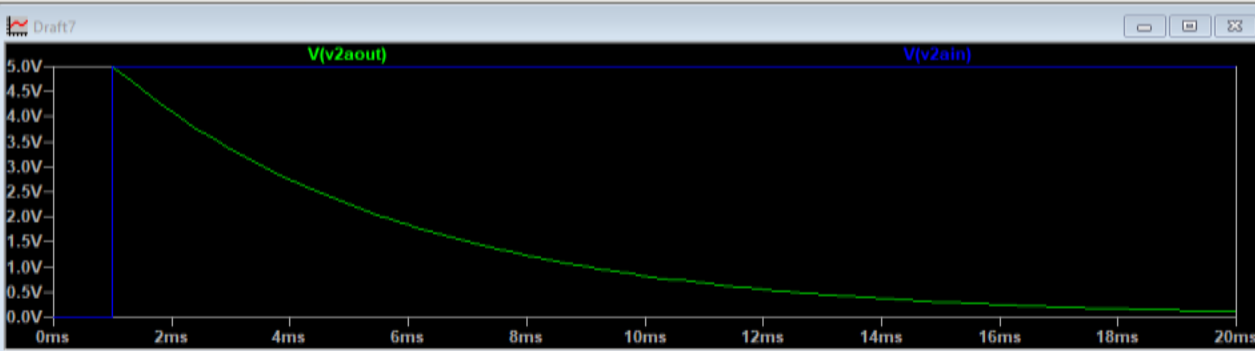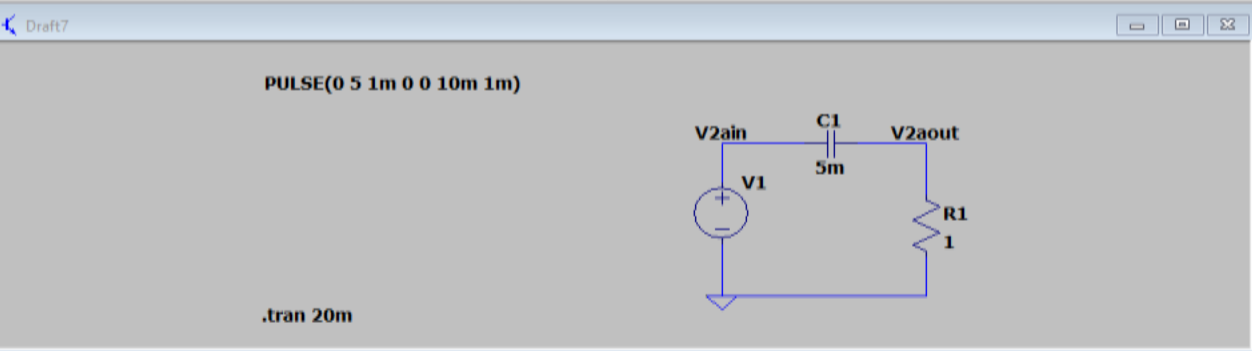

Q2) ii-a,b,c

ii-a)

The input voltage is a unit step function, when a capacitor is discharged, the voltage across the resistor is 5V. However, as the capacitor charges, the voltage across the resistor decreases and eventually becomes almost zero at a very long time.

ii-b)

The input voltage is a square pulse, Initially when the circuit is turned on, the voltage suddenly spikes to 5V as capacitor behaves shorted. Then the cap starts charging and voltage across it starts increasing, thus voltage across resistor decreases. However, as the pulse ends and $V(\text{in})$ becomes 0, the stored energy in the capacitor starts to dissipate. This results in a zero $V(\text{out})$.







ii-c)

The infinite square pulses with peak voltage 5V and minimum voltage 0V, a capacitor charges when the input voltage is 5V and discharges through a resistor when the input voltage is 0V, causing oscillations. Eventually, the capacitor reaches a steady state, resulting in constant maximum and minimum voltages across the resistor for each pulse.

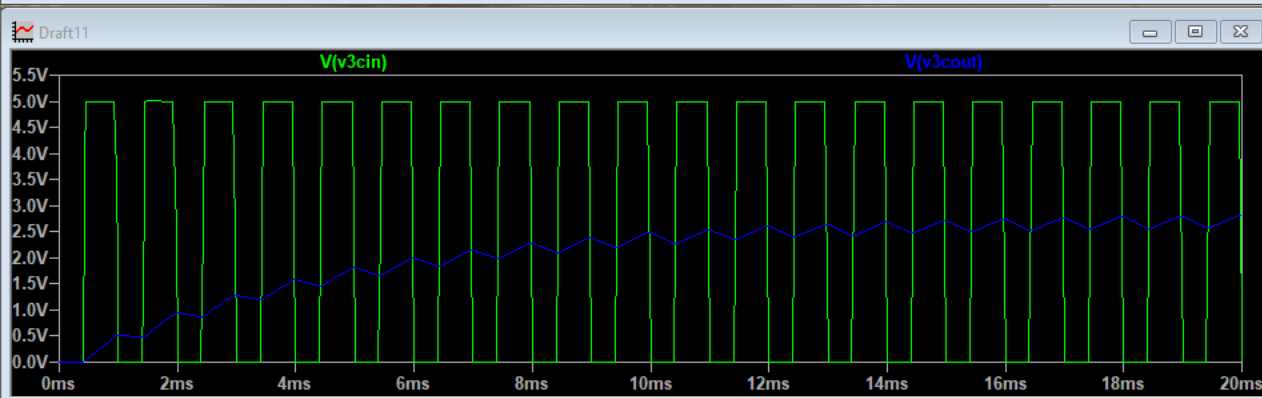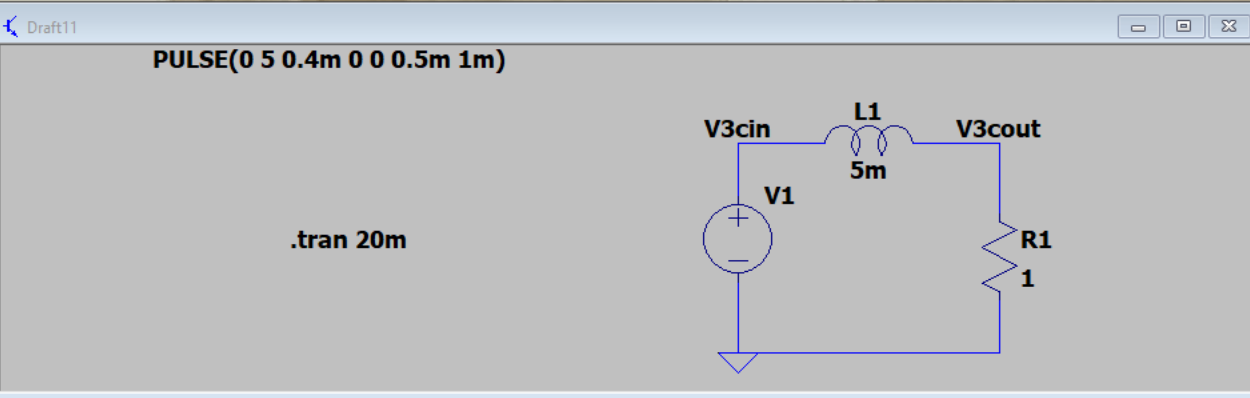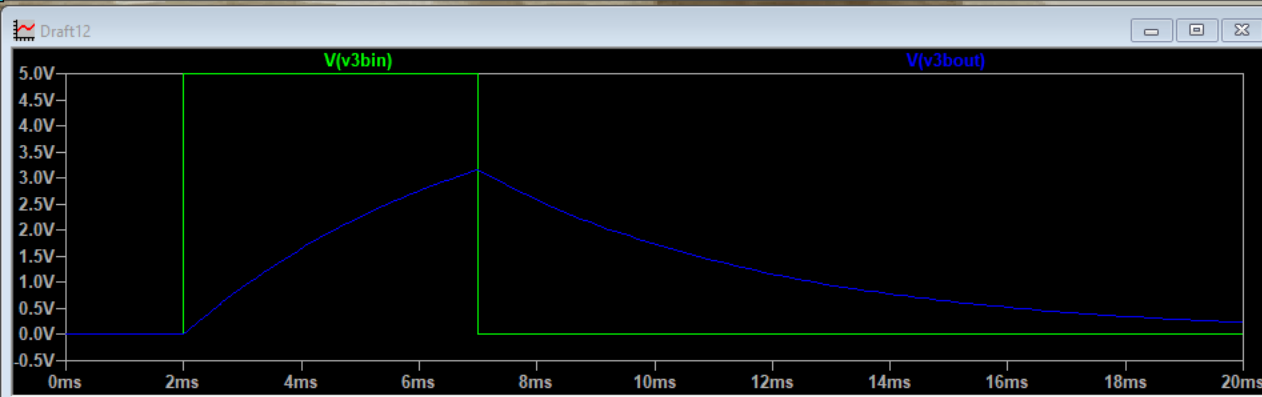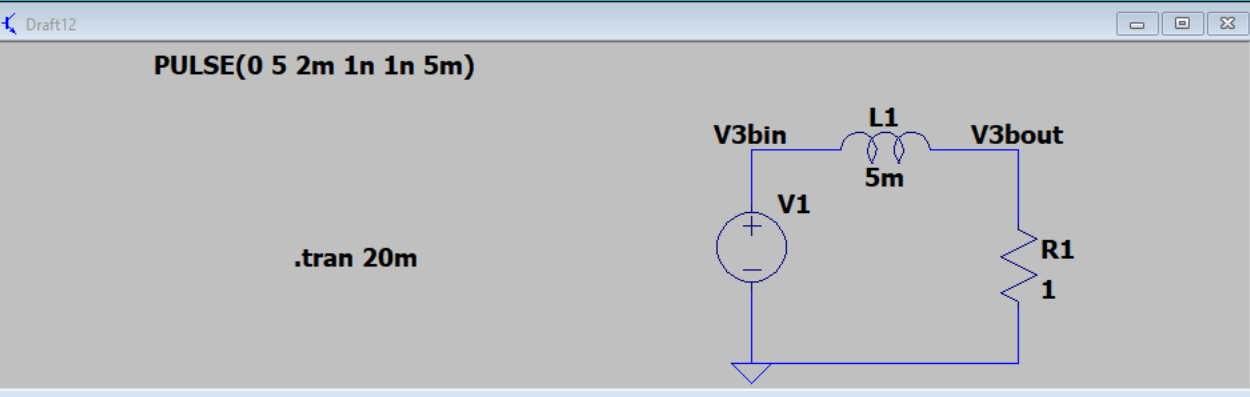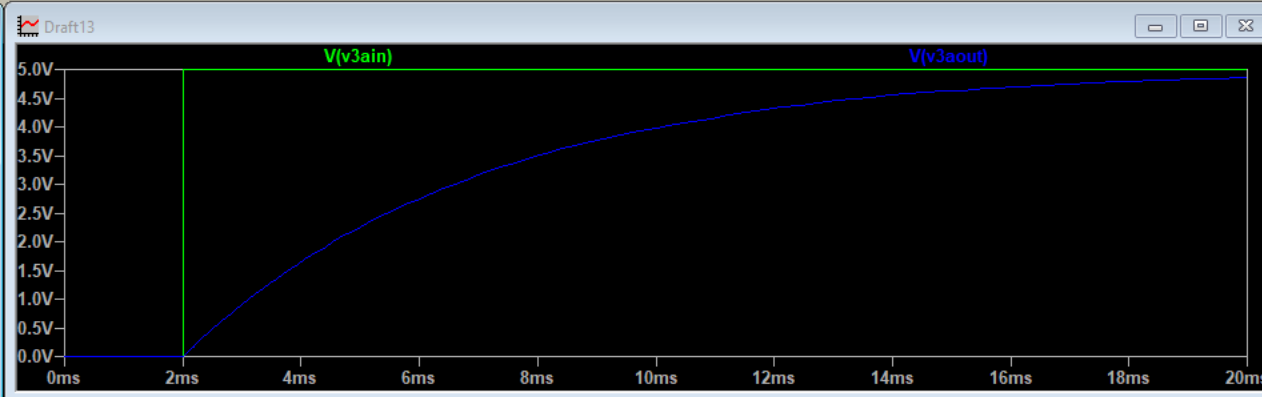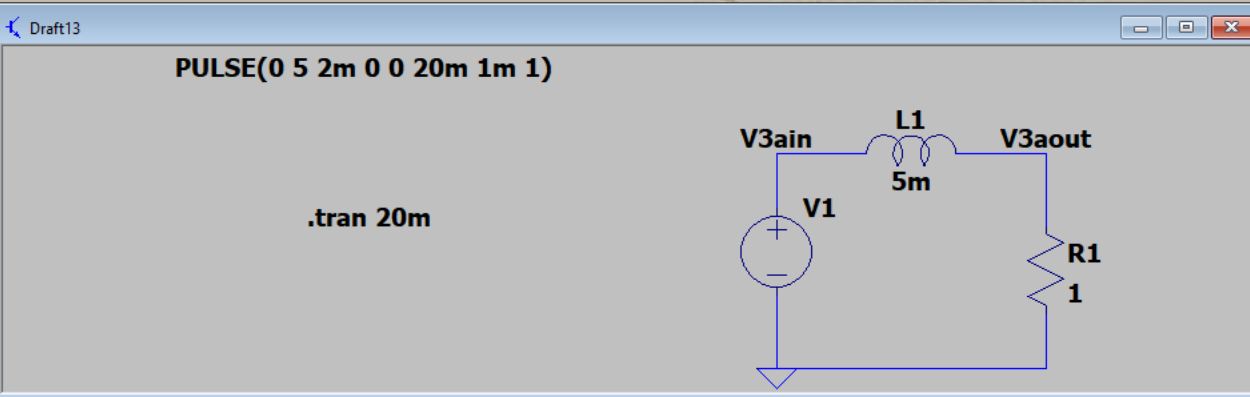Q2) iii-a,b,c



Draft11 Draft11 Draft12 Draft12 Draft13 Draft13



Q2) iii-a,b,c

iii-a)

When a unit step function takes time to increase, the inductor voltage spikes. Initially, the inductor opposes current flow, resulting in zero voltage across the resistor. Voltage across the inductor decreases exponentially, while voltage across the resistor increases over time and reaches a maximum value.







iii-b)

Initially, current and voltage across resistance are zero. Charging inductor increases current and voltage. When the pulse ends, inductor discharges and current decays, causing the voltage across the resistor to decrease and tend to 0.

iii-c)

Infinite square pulses with 5V peak and 0V minimum cause the voltage across the inductor to increase to 5V and voltage across the resistor to start increasing. When the pulse ends, the inductor decays through the resistor, causing the voltage across the resistor to decrease. After several cycles, the maximum and minimum values of $V(\text{out})$ become constant.

Q2) iv-a,b,c

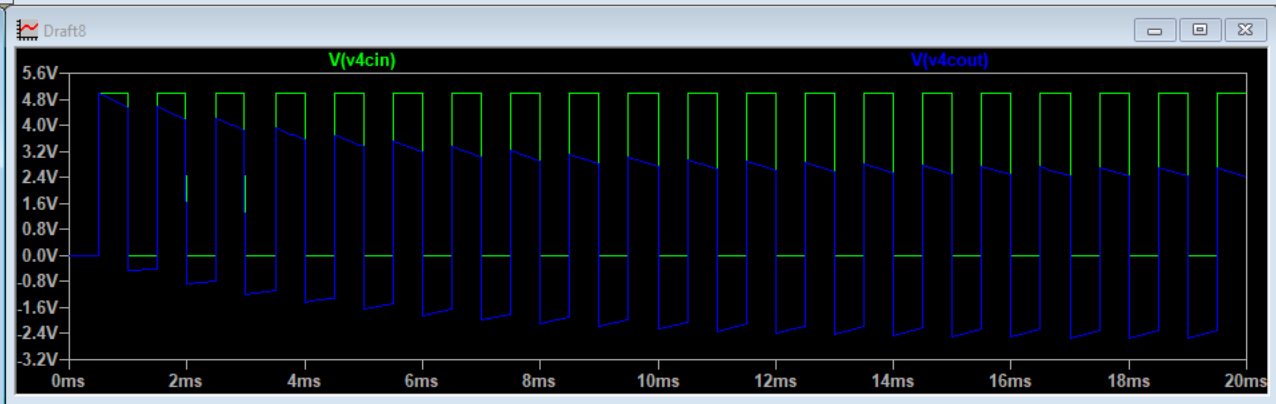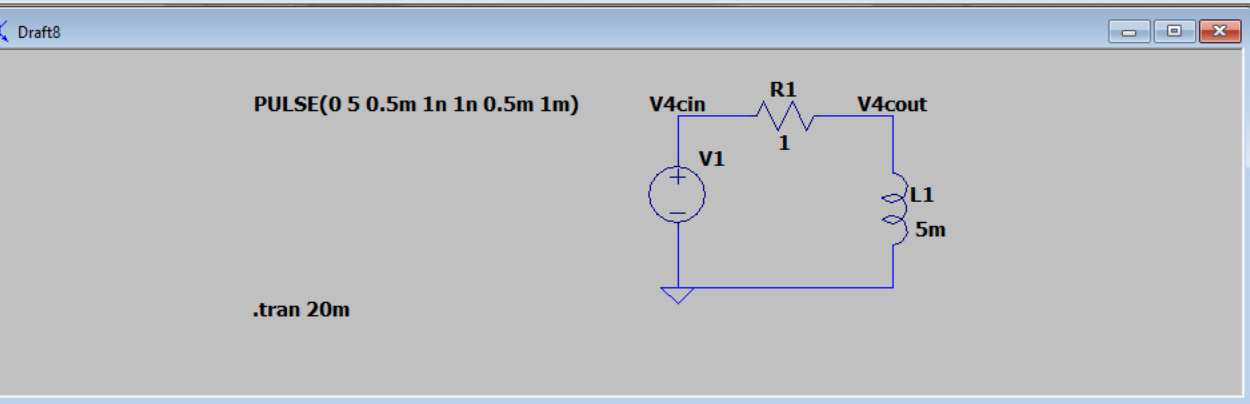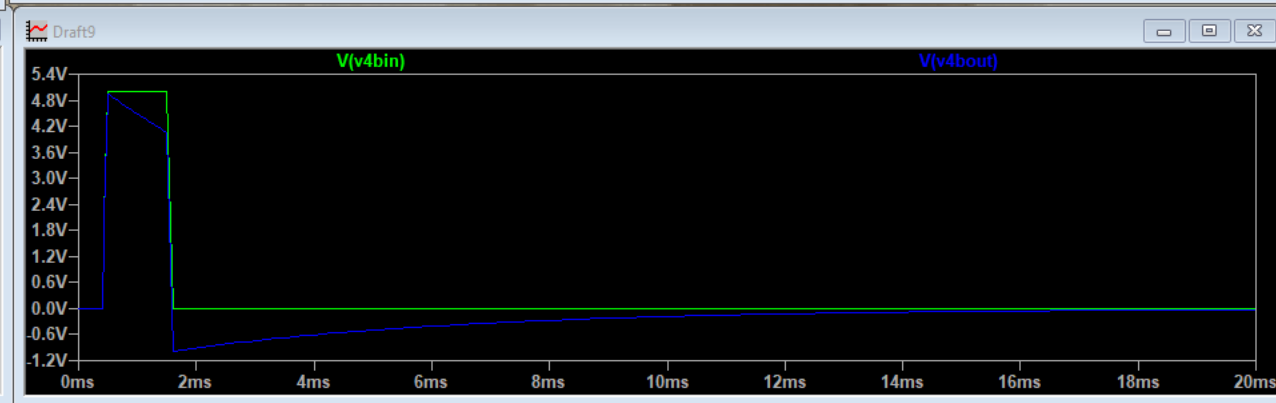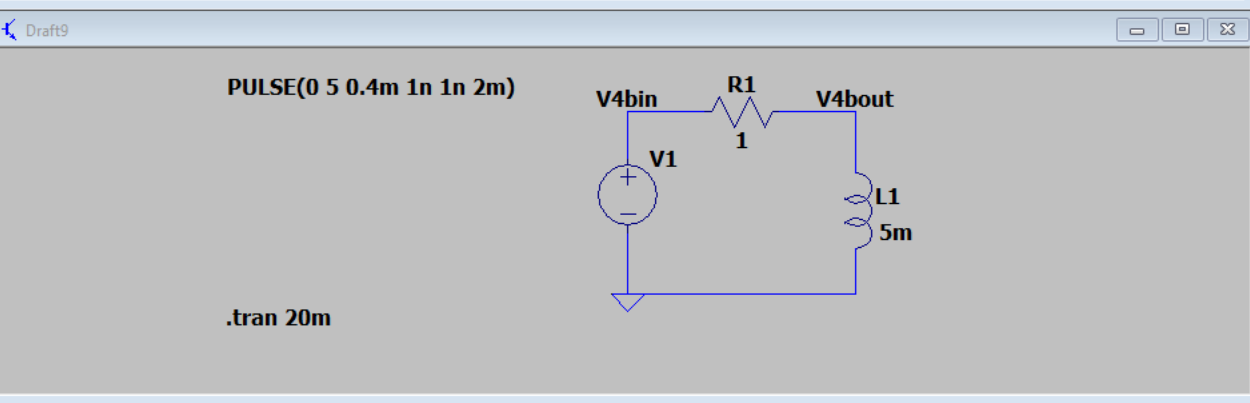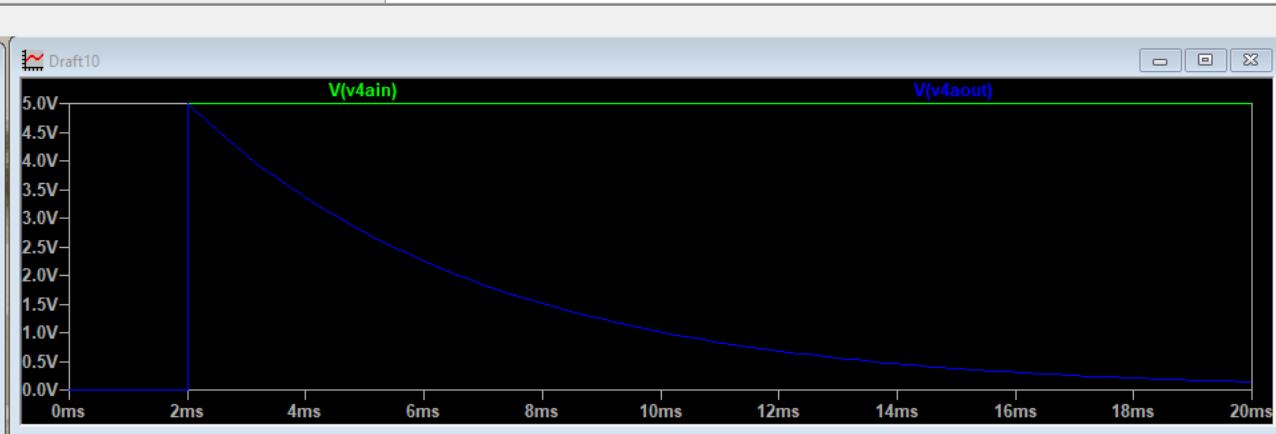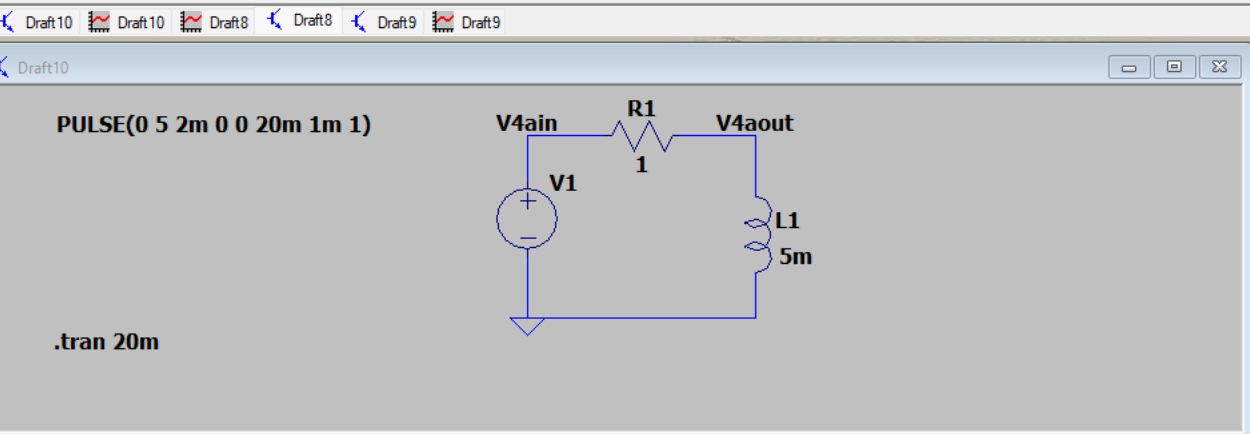

Q2) iv-a,b,c

iv-a)

The voltage across the inductor starts at 5 volts when the voltage across the resistor is zero. As the voltage across the resistor increases, the voltage across the inductor decreases and approaches zero.

iv-b)

At turn on, the voltage across the inductor spikes to 5V, then decreases. When V1 becomes 0, stored energy in the inductor dissipates across resistor, causing current reversal and voltage to tend towards 0.


iv-c)

Infinite square pulses with 5V peak and 0V minimum cause the inductor to have 5V across it and the resistor to have 0V across it. Inductor energy decays through resistor continuously. After several cycles, inductor reaches steady state with constant max and min voltage across it.

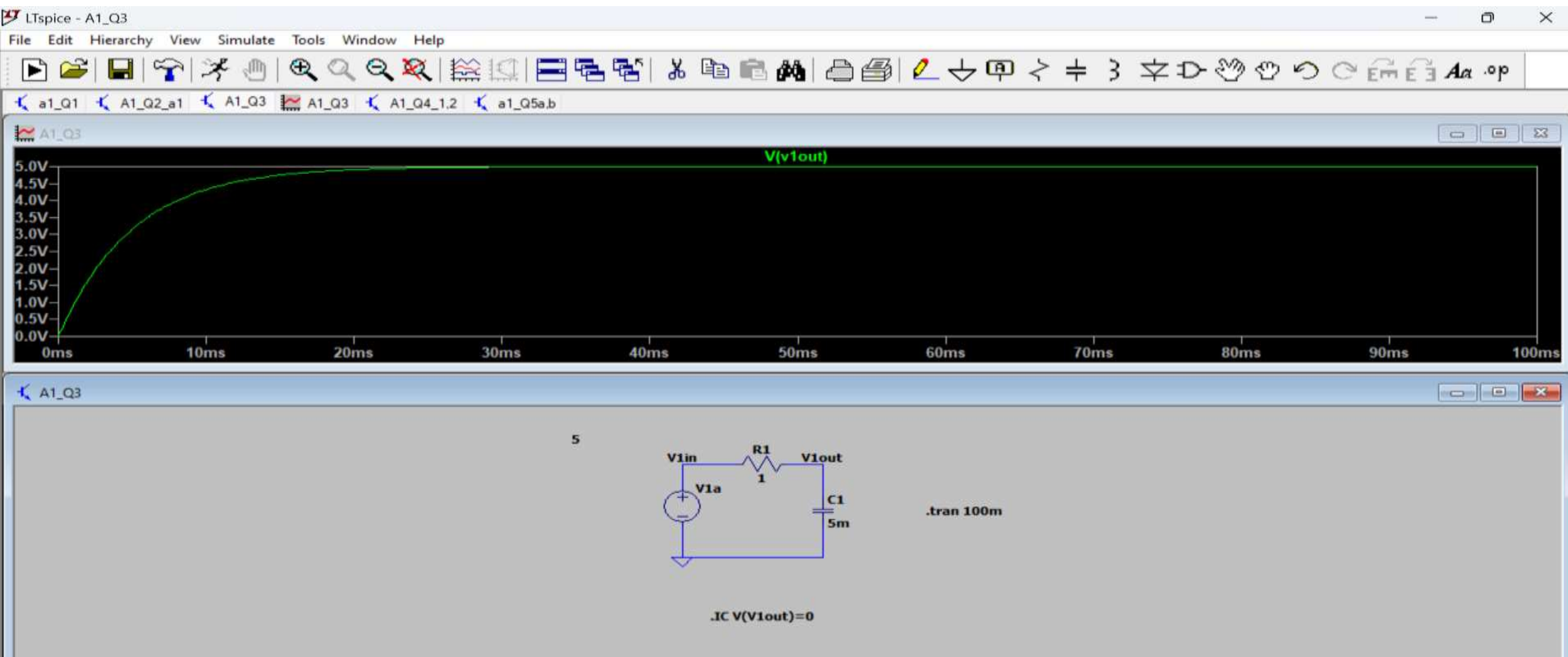Q3a)


Here initially,

voltage across capacitor is zero and gets charged as time passes and reaches saturation voltage of 5 V



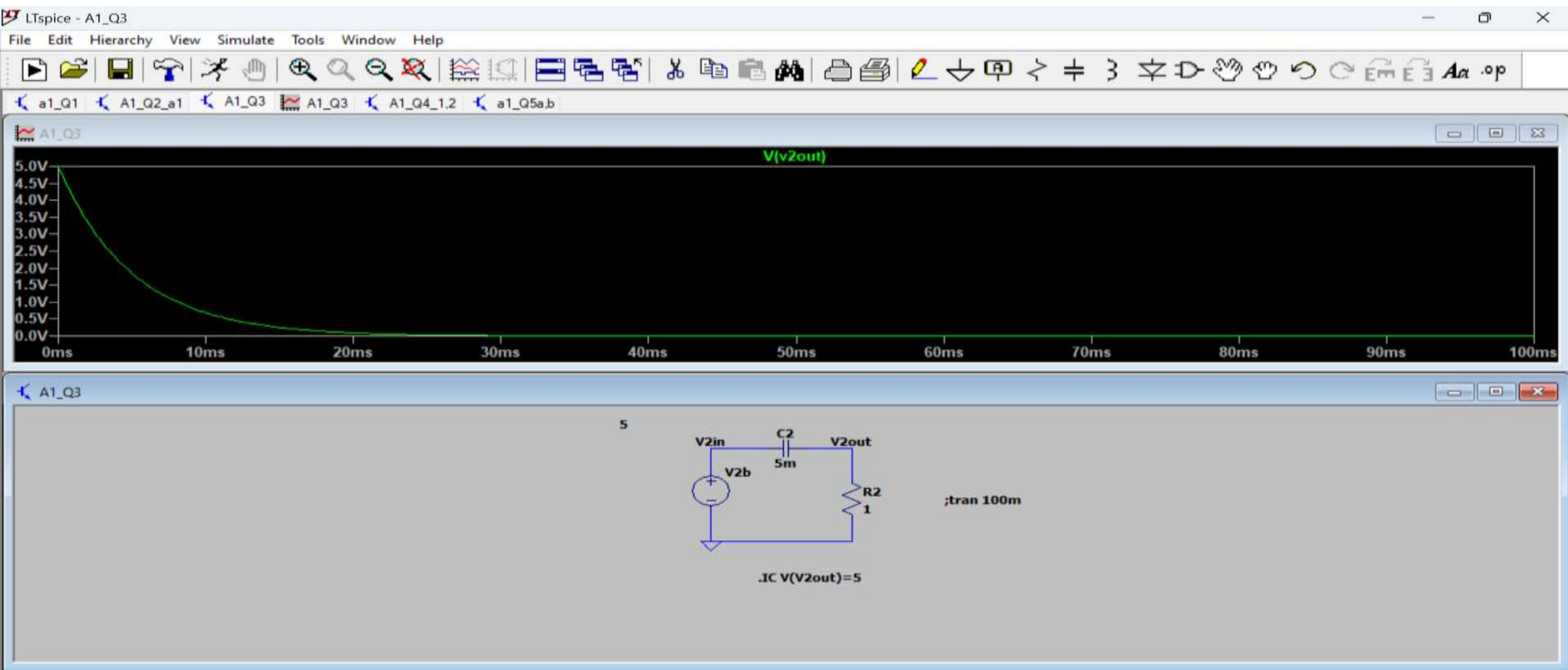
Q3b)

As capacitor is initially discharged, the voltage across resistor is 5 V. As the capacitor charges the voltage across resistor decrease and tends to zero at a very large time



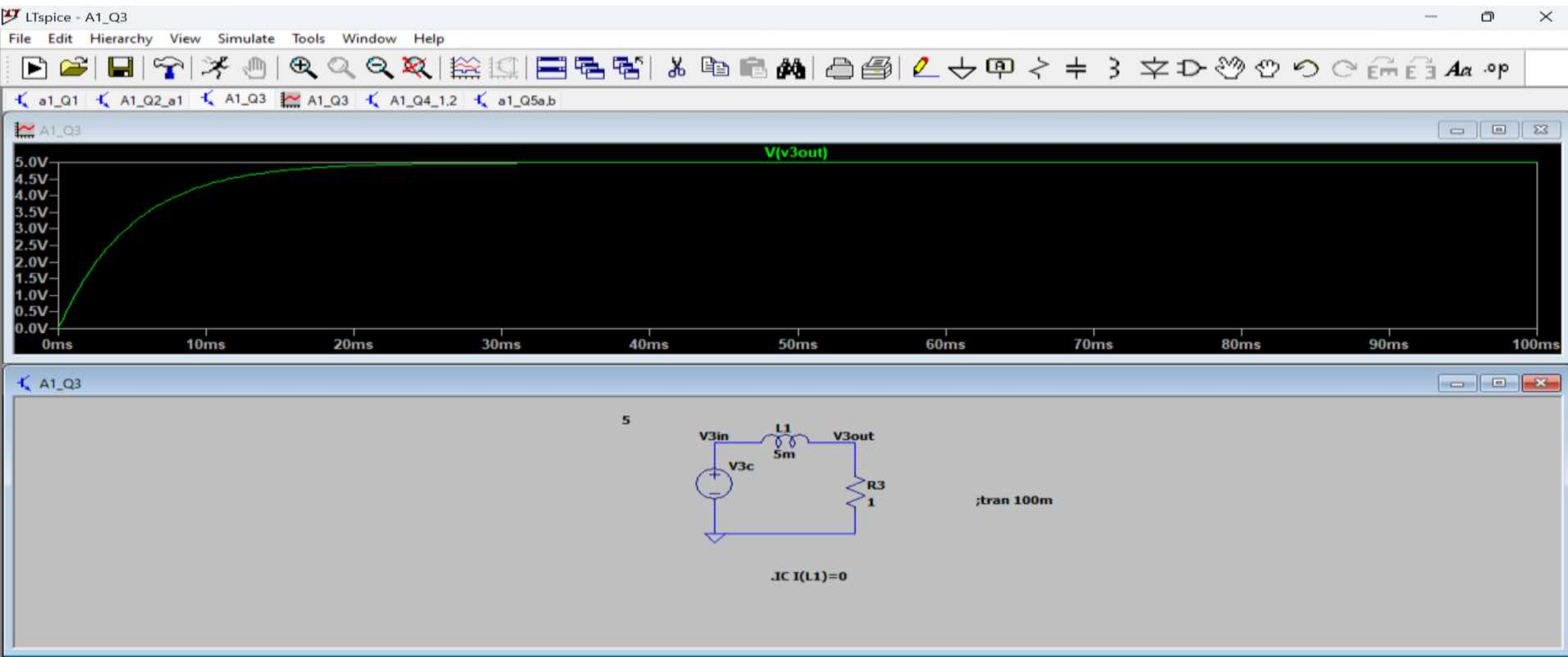
Q3c)

As inductor initially behaves like a broken wire , the current in the circuit is zero, so the voltage across resistor is also 0 V. As the current grows, the voltage across the resistor increases and reaches a saturation value of 5 V.




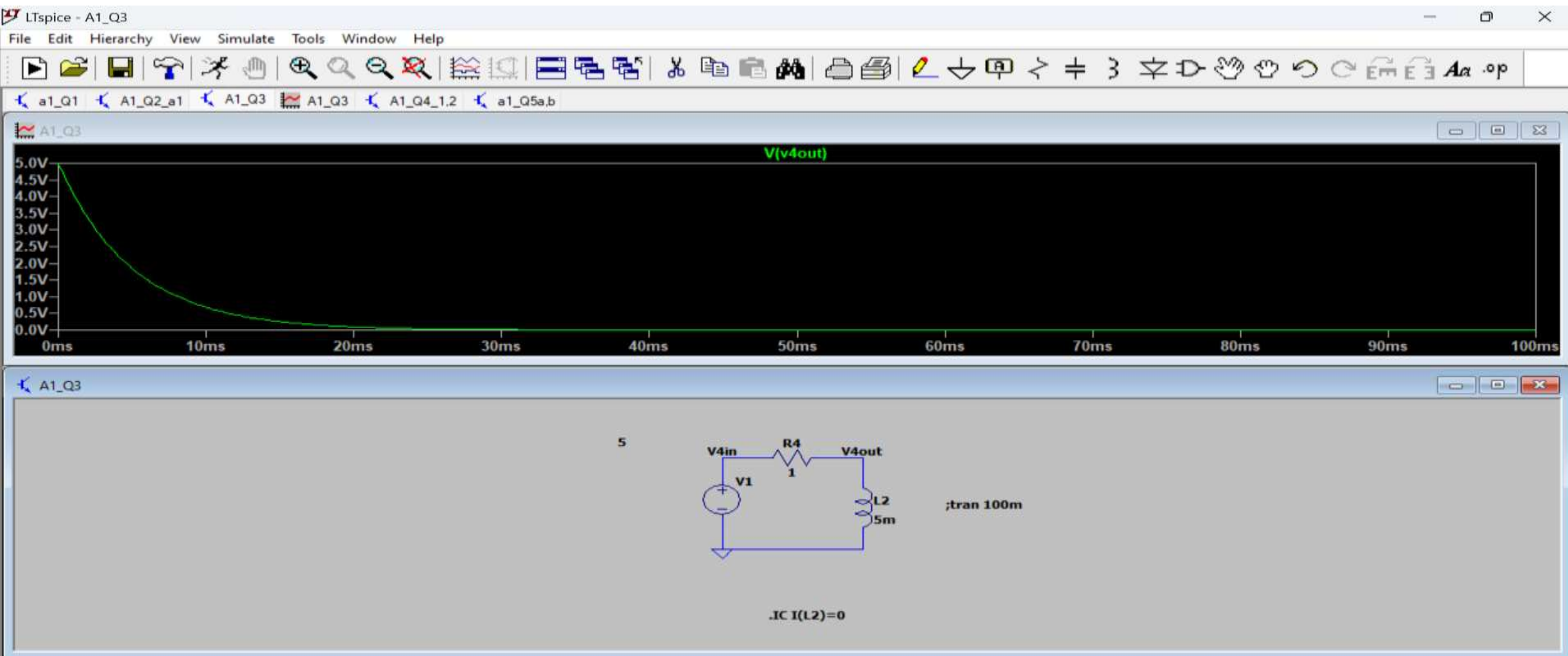Q3d)


The voltage across inductor is equal to $5 - V_r$, where V_r is voltage across resistor. As V_r is zero initially, Voltage across inductor is 5 V. As V_r increases, Voltage across inductor decreases and tends to zero



Q4a)

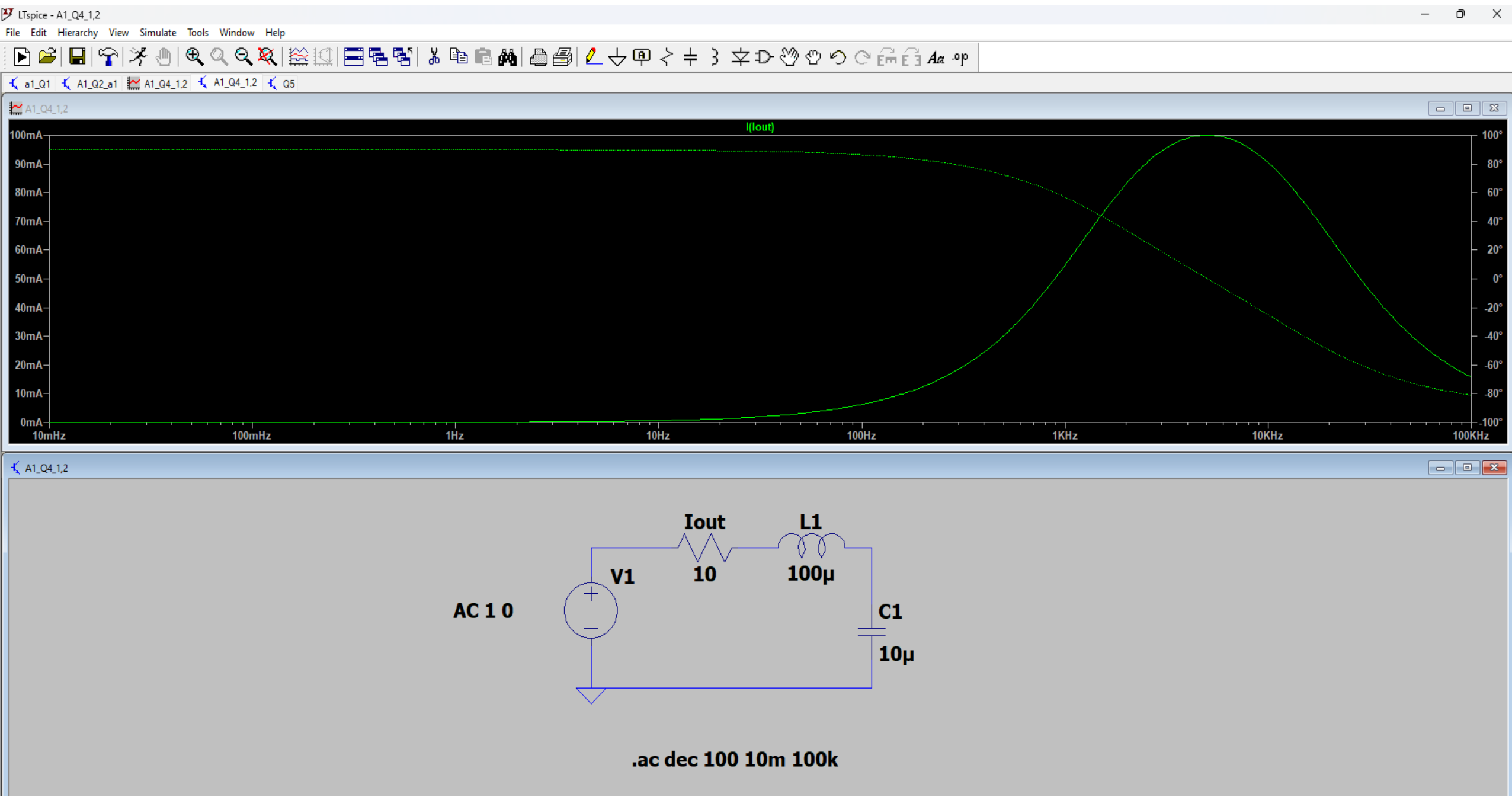

Q4b)

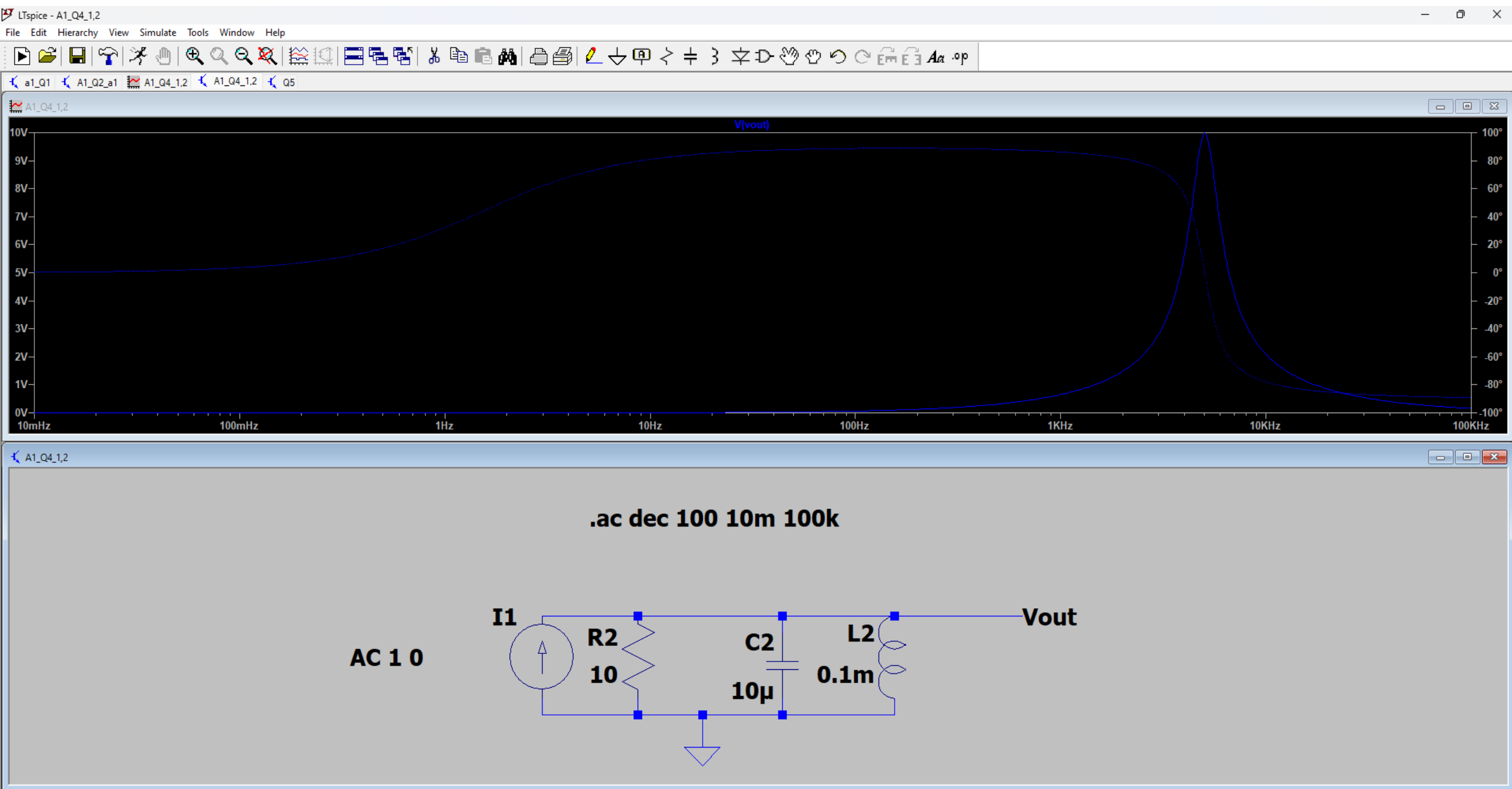

Q5)

Series connection


When Resistance is 0,

The circuit becomes a simple LC circuit with $L=1\text{mH}$ and $C=1\text{mF}$.

The output is that of LC oscillations with $\omega=1/\sqrt{LC}=1000\text{ s}^{-1}$

Since $\omega=1000\text{ s}^{-1}$, Time period is $T=2\pi/\omega=2\pi\text{ ms}$.

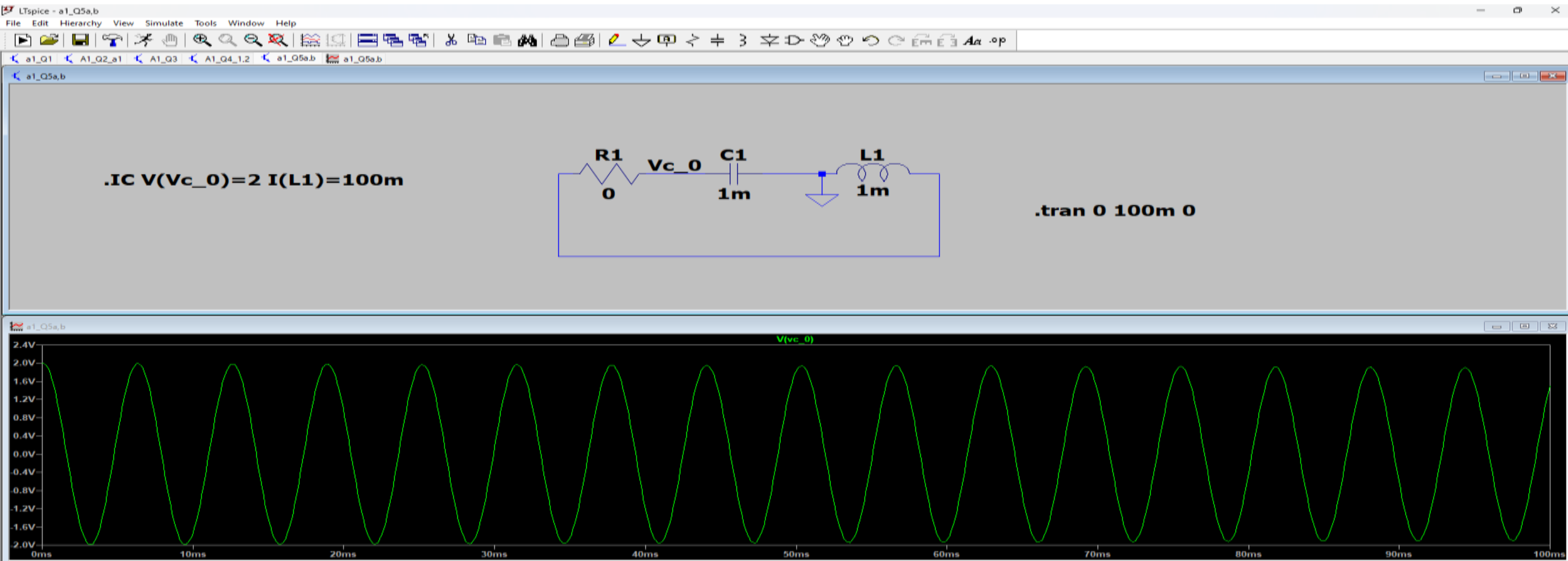
Also since there is no resistance, there is no power dissipated.



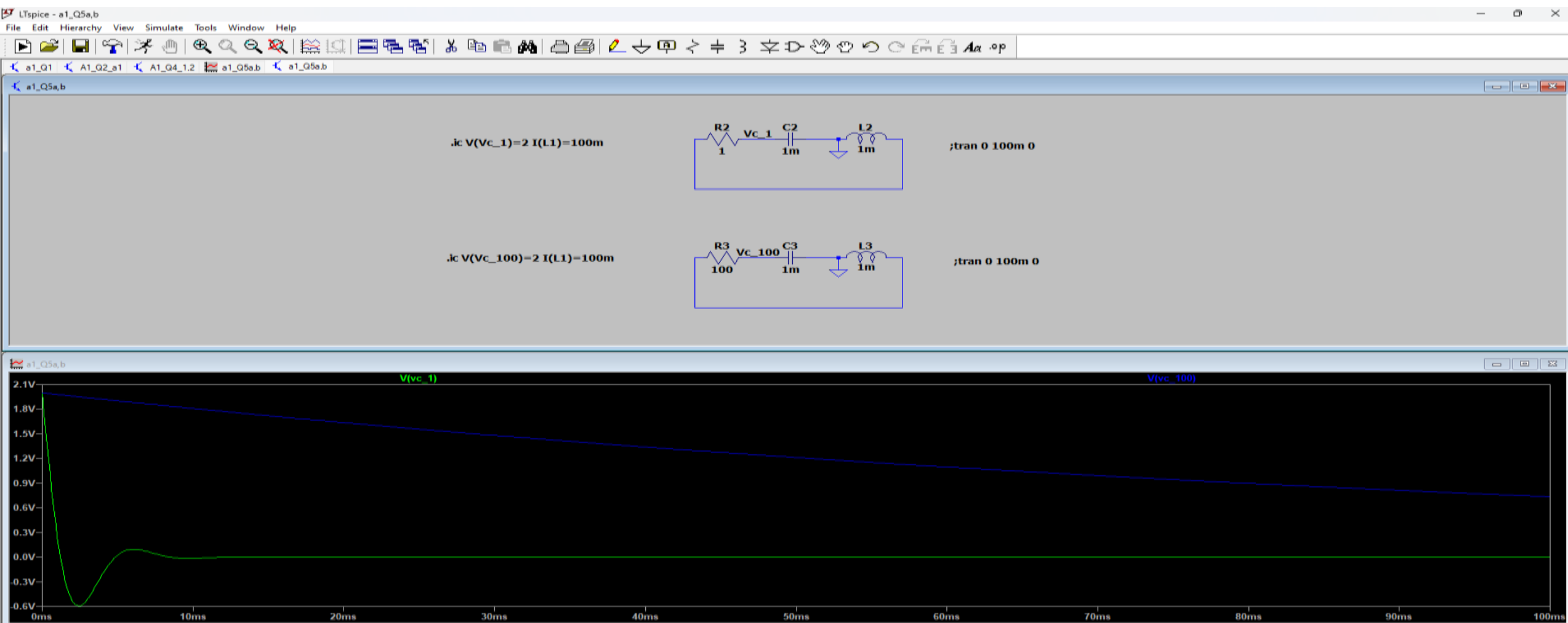Q5)

In $R=1$ case, the damping coefficient $\alpha = 1/2RC = 500$ which is less than $\omega_0 = 1/\sqrt{LC} = 1000$ so it is underdamped. Thus there is mild LC oscillation which eventually disappears as the power dissipates across the resistor.

In $R=100$ case, the damping coefficient $\alpha = 1/2RC = 50000$ which is much lesser than ω_0 so it is overdamped. So here there is an exponential decay of voltage across capacitor.




Q5)

Parallel connection

When Resistance is infinite, current through that wire becomes zero
So we can just remove the wire.

The circuit becomes a simple LC circuit with $L=1\text{mH}$ and $C=1\text{mF}$.
The output is that of LC oscillations with $\omega=1/\sqrt{LC}=1000\text{ s}^{-1}$

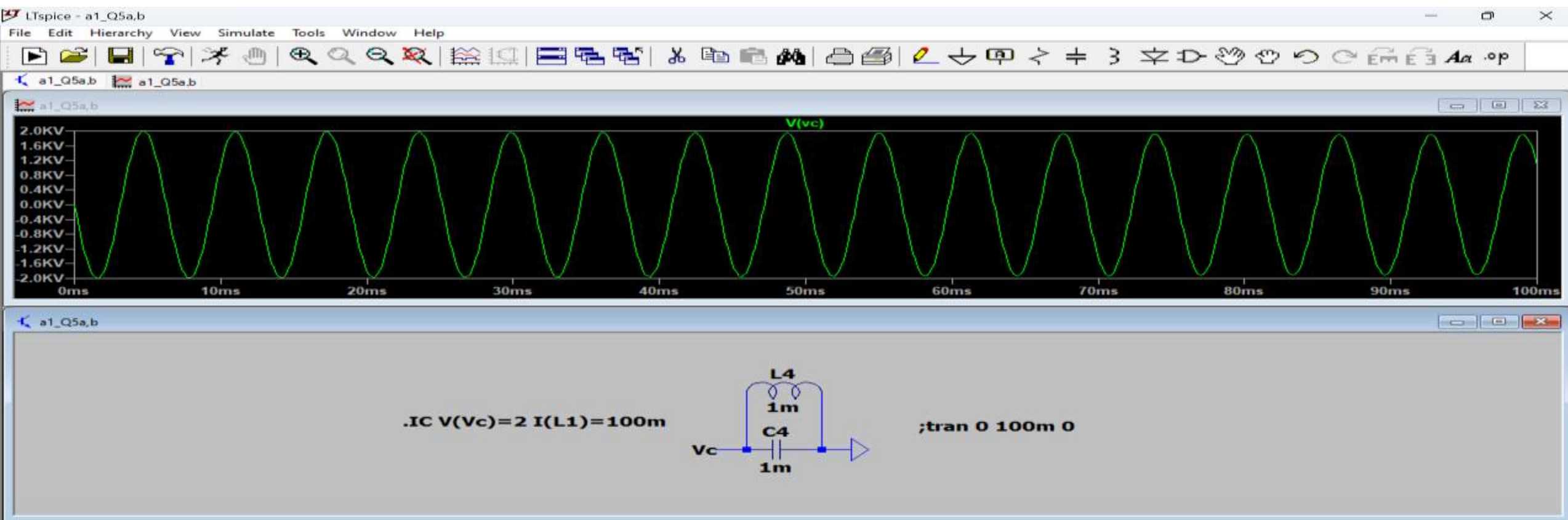Since $\omega=1000\text{ s}^{-1}$, Time period is $T=2\pi/\omega=2\pi\text{ ms}$.



Q5)

In the $R=1$ case, the damping coefficient $\alpha = 1/2RC = 500$ which is less than $\omega_0 = 1/\sqrt{LC} = 1000$ so it is underdamped. Thus there is mild LC oscillation which eventually disappears as the power dissipates across the resistor.

In the $R=100$ case, the damping coefficient $\alpha = 1/2RC = 5$ which is lot lesser than ω_0 so it is very underdamped. So here there is almost perfect LC oscillation at the start which decays overtime and gets imperfect eventually

