

# Lab Report

## Lab Session-8

**MATHEW M PHILIP EE22BTECH11211**

**JAY VIKRANT EE22BTECH11025**

**AIM:** Build an Asynchronous counter and verify the functionality. You may have to use Arduino to get low frequency clock to verify.

**COMPONENT:** LED(x4), Wires, Arduino UNO, IC 7476

**THEORY:** The counter is an electronic device that can count from 0 to 15. We use an asynchronous counter to build this. An asynchronous counter also known as a ripple counter is a type of counter that can count in a binary sequence using a series of flip-flops. Unlike a synchronous counter, where a common clock signal is fed to all the flip-flops, an asynchronous counter relies on the output of the previous flip-flop to act as the clock to the next flip-flop.

The basic building block of an asynchronous counter is JK flip-flop: it has two inputs (J input and a K input) and a clock input. The clock input controls when the flip flop updates its outputs based on the input data. The output of one flip-flop is connected to the clock input of the next flip-flop in sequence.

To create an n-bit counter, n flip-flops are to be connected in series. The output of the first flip-flop represents the Least Significant Bit (LSB) and the output of the last flip-flop represents the Most Significant Bit (MSB). This causes a ripple effect where each flip-flop changes its state one after the other, resulting in a binary counting sequence.

The JK flip-flops must be used in a toggle state to get the required output. So, we connect both J and K inputs to the "1" or the high state. So, in each negative edge pulse transition the output of the D flip-flop is the complement of the previous output.

$$Q(n + 1) = Q'(n)$$


The outputs of each of the flip-flop is clock wave having frequency half of that of the clock input of the respective flip-flop. i.e., If the frequency of the clock=f.

The frequency of the first output wave=f/2

The frequency of second output wave= $f/4$

The frequency of third output wave= $f/8$

 
The frequency of fourth output wave= $f/16$



The above is the timing diagram for the asynchronous ripple counter. We can see that for each output the frequency gets halved or the time-period doubles.

Table 1: Truth table for a 4-bit synchronous counter using JK flip-flops


Clock	Q0	Q1	Q2	Q3	Next State
0	0	0	0	0	0000
1	0	0	0	1	0001
1	0	0	1	0	0010
1	0	0	1	1	0011
1	0	1	0	0	0100
1	0	1	0	1	0101
1	0	1	1	0	0110
1	0	1	1	1	0111
1	1	0	0	0	1000
1	1	0	0	1	1001
1	1	0	1	0	1010
1	1	0	1	1	1011
1	1	1	0	0	1100
1	1	1	0	1	1101
1	1	1	1	0	1110
1	1	1	1	1	1111

 

**PROCEDURE:** Firstly, we write the code in Arduino IDE for input clock. The clock is made using example code from Files>example>Basics>Blink in the IDE. In the code High voltage is set for pin(7) on Arduino uno, then the delay of High voltage and LOW voltage is set to 10000 units as each unit is a millisecond, for a time period of 10 seconds. Thus, resulting in 0.1 Hz square waves.

Now, the following wiring is done to achieve the desired output.

 1. Connect the clock (i.e pin (7)) output of the Arduino to the clock input of first JK flip-flops.
2. Connect the reset and clear input of all four JK flip-flops to  $V_{cc}$ .
3. Connect the J and K inputs of the first JK flip-flop to  $V_{cc}$ .
4. Connect the  $Q'$  output of the first JK flip-flop to the CLK input of the second JK flip-flop of the same IC7476.
5. Connect the  $Q'$  output of the second JK flip-flop of the first IC7476 to the clock of the first JK flip-flop of the second IC7476.
6. Connect the  $Q'$  outputs of all four JK flip-flops to the LEDs.



The clock has a time period of 20 seconds.

```
Blink | Arduino 1.8.19
File Edit Sketch Tools Help

Blink $
/*
  Blink

  Turns an LED on for one second, then off for one second, repeatedly.
*/

// the setup function runs once when you press reset or power the board
void setup() {
  // initialize digital pin LED_BUILTIN as an output.
  pinMode(7, OUTPUT);
}

// the loop function runs over and over again forever
void loop() {
  digitalWrite(7, HIGH); // turn the LED on (HIGH is the voltage level)
  delay(1000);           // wait for a second
  digitalWrite(7, LOW);  // turn the LED off by making the voltage LOW
  delay(10000);          // wait for a second
}

Done compiling.


Sketch uses 924 bytes (2%) of program storage space. Maximum is 32256 bytes.
Global variables use 9 bytes (0%) of dynamic memory, leaving 2039 bytes for local variables. Maximum is 2048 bytes.

17 Arduino Uno on COM8
```


## RESULT:

The following result was observed from t=0 to t=300 seconds,


0000

 


0010

 

1000

 


1010

 





0100

 


0110

 


1100

 


1110

 


0001

 


0011

 


1001

 


1011

 


0101

 


0111

 

1101

 



1111

 

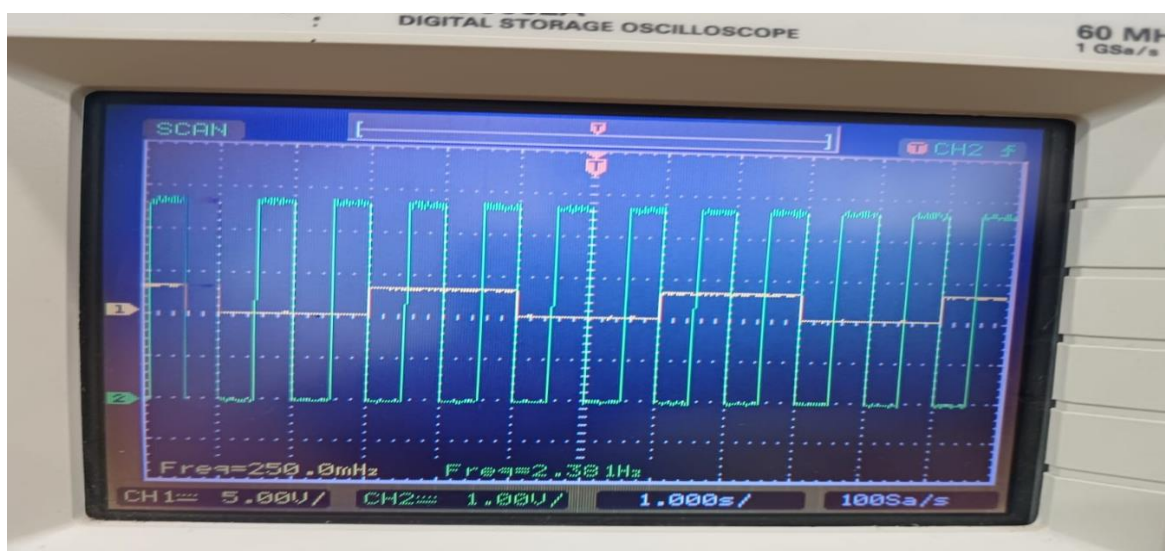Also, the following result was seen in the oscilloscope for each output (i.e the LED from left to right)





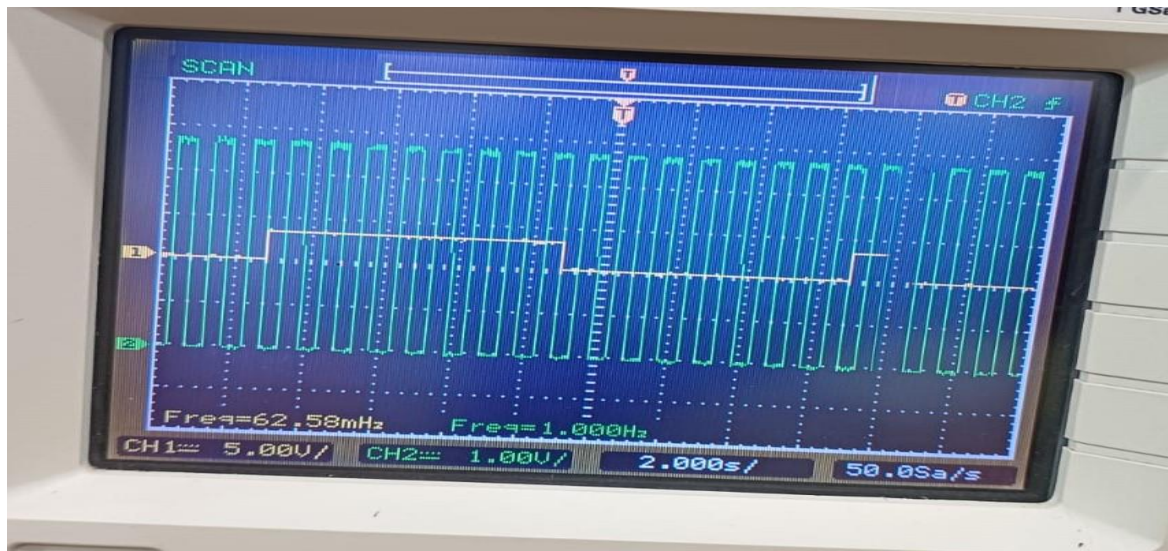

We observe that frequency is halved for every output from left to right.